

Digital Integrated Circuits

Homework #2

Due 2 hours before the next lecture

Problem 1: Equivalent Resistance

Consider NMOS device with $W = 240\text{nm}$ and $L = 100\text{nm}$ (effective $L = 70\text{nm}$). Using the resistor averaging technique discussed in class, and parameters below, calculate R_{on} as V_{DD} changes from 0.4V to 1V in steps of 0.2V . Compare the results of your hand calculations with simulation results in Table 2.

Use following parameters for hand calculations:

$$\lambda = 0.795 \text{ V}^{-1}$$

$$k' = 129.5 \mu\text{A}/\text{V}^2$$

$$L_{\text{eff}} = 70 \text{ nm}$$

$$V_{\text{th}} = 0.168 \text{ V}$$

$$V_{\text{dsatn}} = 0.3 \text{ V}$$

Table 2: R_{on} (Analytical vs. Simulation)

R_{on}	$I_{\text{DSAT}} (\mu\text{A})$	Analytical Model (R_{eq})	Simulation
			2-point avg
$V_{\text{DD}} = 0.4\text{V}$			27.8 k Ω
$V_{\text{DD}} = 0.6\text{V}$			9.0 k Ω
$V_{\text{DD}} = 0.8\text{V}$			6.5 k Ω
$V_{\text{DD}} = 1.0\text{V}$			5.0 k Ω

Problem 2: Inverter in Subthreshold

The inverter below, operates with $V_{\text{DD}} = 0.175\text{V}$ and is composed of $V_{\text{Tn}} = |V_{\text{Tp}}| = 0.20\text{V}$ devices. They can be described by the subthreshold voltage-current relation. The devices have identical I_s and n , ($n=1.5$ and $kT/q=26\text{mV}$).

 


Figure 2: Inverter in Subthreshold.

- 2A** Calculate the **switching threshold** (V_M) of this inverter.
If the equation is difficult to solve, plot both sides and find the intersection point for a numerical answer.
- 2B** Calculate V_{IL} and V_{IH} of the inverter.
You may find piecewise-linear approximation helpful.

Problem 3: MOS Capacitance

Use the following table.

Assumptions:

$|V_{TH}| = 0.2V$ for both NMOS and PMOS

For the purpose of capacitance calculation (only), treat velocity saturation as saturation

Param.	C_{ox} [fF/ μm^2]	C_o [fF/ μm]
NMOS	15	0.27
PMOS	14	0.25

- 3A** What is the t_{ox} (nm) of the NMOS transistor?
- 3B** Consider a PMOS biased with $V_G = V_D = V_S = V_B = 0V$
 Assume $W = 480$ nm, $L = 120$ nm, $L_D = L_S = 240$ nm
 Calculate the following capacitances:
 (B1) Gate-to-Channel capacitance (C_{GC})
 (B2) Gate-to-Source capacitance (C_{GS})
- 3C** Consider an NMOS biased with $V_G = V_D = 0.8V$, $V_S = V_B = 0V$
 Assume $W = 240$ nm, $L = 120$ nm, $L_D = L_S = 240$ nm
 Calculate the following capacitances:
 (C1) Gate-to-Channel capacitance (C_{GC})
 (C2) Gate-to-Source capacitance (C_{GS})

Clearly indicate your final formulas and circle/highlight your answers.

Problem 4: Computing Capacitance

Consider the circuit in Figure 4. Calculate the total equivalent capacitance on node X as it charges from 0 to $V_{DD}/2$.

 



Figure 4

You can use the following capacitance values in your calculations:

$$\begin{aligned} C_{db_NMOS} &= 0.06 \text{ fF}, & C_{db_PMOS} &= 0.10 \text{ fF} \\ C_{gd_NMOS} &= 0.14 \text{ fF}, & C_{gd_PMOS} &= 0.26 \text{ fF} \\ C_{g1} &= 0.16 \text{ fF}, & C_{g2} &= 0.30 \text{ fF} \end{aligned}$$

 Problem 5: VTC

Consider the inverter below, with the input at the gate of the PMOS and a diode-connected NMOS.



Device parameters:

$$\begin{aligned} V_{TN} &= 0.2 \text{ V}, & V_{TP} &= -0.2 \text{ V} \\ V_{DSATN} &= |V_{DSATP}| = 0.3 \text{ V} \\ k'_n &= 130 \mu\text{A/V}^2 \\ k'_p &= -100 \mu\text{A/V}^2 \\ (W/L)_A &= 1 \\ (W/L)_B &= 4 \\ \lambda &= 0, \gamma = 0 \text{ for both transistors} \\ V_{DD} &= 1 \text{ V} \end{aligned}$$

(a) Calculate V_Y for $V_{IN} = 0 \text{ V}$.

$V_Y =$

(b) Calculate V_Y for $V_{IN} = V_{DD}$.

$V_Y =$

(c) Ignoring the results from (a) and (b), calculate switching threshold V_M for the inverter. Is V_M expected to be greater or smaller than 0.5V ? (circle the correct answer)

$V_M > 0.5 \text{ V}$

$V_M < 0.5 \text{ V}$

Briefly explain why:

What are the modes of operation for M_A and M_B ?

M_A :	M_B :
---------	---------

Calculate the value of V_M .

$V_M =$
