



21

 
Problem 1: Gate Sizing of a Multi-Stage Network

Figure 1

Consider the multi-stage logic shown in Figure 1. The numbers represent relative input gate capacitance. For example, the inverter with "1" has input capacitance of C_{in} , the inverter with "21" has input capacitance of $21C_{in}$ because it is 21 times as wide. Output is loaded with $60C_{in}$.

- 1A** Find the minimum delay from input to output using logical effort.
- 1B** Find the size of the NAND and NOR gates x and y (NAND has input capacitance $x C_{in}$ and NOR has input capacitance $y C_{in}$) that minimize the delay from input to output.

$$g_{inv} = 1 \quad h_1 = \frac{x}{1}$$

$$g_{NAND} = \frac{4}{3} \quad h_2 = \frac{y}{x}$$

$$g_{inv} = \frac{1}{3} \quad h_3 = \frac{60}{y}$$

$$P_{inv} = 1$$

$$P_{NAND} = 2 \quad P_{NOR} = 2$$

$$1A \quad t = (GBH)^{\frac{1}{3}} \quad b = \frac{60+21}{60} = B = 1.35$$

$$= \left(1 \cdot \frac{4}{3} \cdot \frac{1}{3} \cdot 1.35 \cdot \frac{60}{1}\right)^{\frac{1}{3}} = (63.572)^{\frac{1}{3}} = 3.99$$

$$\text{Minimum Delay: } D_{min} = N \cdot t + P = \sum (g_i h_i + p_i)$$

$$= 3 \cdot 3.99 + (1 + 2 + 2) = 16.97$$

$$1B: \quad y: \text{NOR: } \frac{5}{3} \cdot \frac{60}{3.99} = 25.06 \quad C_{in}$$

$$x: \text{NAND: } \frac{4}{3} \cdot \frac{25.06}{3.99} = 8.37 \quad C_{in}$$


Problem 2: CMOS Logic & Logical Effort

- (a) Design $F = \overline{A + BC + D}$ in Static CMOS. Draw the schematic and size all the transistors such that the worst-case resistance is equal to that of a unit-sized inverter ($W_P:W_N = 2:1$).

(draw your initial circuit below)


(revise your circuit as to minimize delay when inputs transition in the following order: A, C, D, B)

$$W_P:W_N = 2:1$$

 

$$P = \frac{b + (1 + 2 + 1)}{3} = \frac{10}{3}$$

\Rightarrow

 

$$P = \frac{b + b + (1 + 2 + 1)}{3} = \frac{16}{3}$$

- (b) Find the logical effort for all the inputs in your design in part (a)?

$g_A =$
$g_B =$
$g_C =$
$g_D =$

$$g_A = \frac{7}{3}$$

$$g_B = \frac{8}{3}$$

$$g_C = \frac{8}{3}$$

$$g_D = \frac{7}{3}$$

Problem 2: Sizing for Performance and Energy

Q3

- a. Pick the best sizing factors S_2 and S_3 to minimize propagation delay from In to Out . What is the minimum delay (in terms of t_{p0})?

 


Fig. 3a

$S_2 =$	4	$S_3 =$	27
$t_p =$	12 t_{p0}		

$$\bar{f} = \frac{C_L}{C_{in}} = 27$$

$$f^{\#} = (27)^{\frac{1}{3}} = 3$$

$$\begin{aligned} S_2 &= 3^2 = 9 \\ S_3 &= 3^3 = 27 \end{aligned}$$

$$t_p = N t_{p0} (1 + \sqrt[N]{f}) = 3 \cdot t_{p0} (1 + 3) = 12 t_{p0}$$

- b. Pick the best sizing S_2 and S_3 to minimize energy consumption. You may assume square wave input with period T . What is the total energy taken from V_{DD} (ignore energy for driving the input In) for a full cycle ($0 \rightarrow 1, 1 \rightarrow 0$)?

$S_2 =$	1	$S_3 =$	1
$E_{cycle} =$	32C V_{DD}^2		

when they are all 1, i.e. $S_2 = S_3 = 1$

$$\begin{aligned} C_{tot} &= C_{int, s1} + C_{gate, s2} + C_{int, s2} + C_{gate, s3} + C_{int, s3} + C_L \\ &= 1 + 1 + 1 + 1 + 1 + 27 \\ &= 32C \end{aligned}$$

$$E_{cycle} = 32C V_{DD}^2$$

 


Fig. 3c

$$\begin{aligned} S_2 &= 2.8379 \\ S_3 &= 5.0538 \\ t_p &= 17.51 t_{p0} \end{aligned}$$

$$\frac{1}{s_2} (s_3 + 3)$$

$$4s_3^{-1}$$

$$(s_3 + 3) s_2^{-1}$$

$$-(s_3 + 3) s_2^{-2}$$

$$t_p = \left(1 + s_2\right) + \left(1 + \frac{s_3 + 3}{s_2}\right) + \left(1 + \frac{9}{s_3}\right) + \left(1 + \frac{64}{9}\right)$$

Taking partial derivative with respect to s_2 and s_3

$$s_2: 1 - \frac{s_3 + 3}{s_2^2} \Rightarrow 1 = \frac{s_3 + 3}{s_2^2} \quad \left(\frac{s_3}{9}\right)^2 = s_3 + 3$$

$$s_3: \frac{1}{s_2} - \frac{9}{s_3^2} \Rightarrow \frac{1}{s_2} = \frac{9}{s_3^2} \quad 9s_2 = s_3^2 \quad s_2 = \frac{s_3^2}{9}$$

$$s_3 \approx 5.0538 \quad s_2 = 2.8379$$

$$t_p = \left[\left(1 + 2.8379\right) + \left(1 + \frac{5.0538}{2.8379}\right) + \left(1 + \frac{9}{5.0538}\right) + \left(1 + \frac{64}{9}\right) \right] t_{p0}$$

$$= 17.51 t_{p0}$$