

Digital Integrated Circuits

Homework #4

Due 2 hours before the next lecture

$$P(B+C=1) = P(B=0) \cdot P(C=1) = \frac{3}{4} \cdot \frac{1}{3} = \frac{1}{4}$$

$$P(B=1) \cdot P(C=0) = \frac{1}{4} \cdot \frac{2}{3} = \frac{1}{6}$$

$$P(B=1) \cdot P(C=1) = \frac{1}{4} \cdot \frac{1}{3} = \frac{1}{12}$$

$$= \frac{1}{2}$$

Problem 1: Finding α

Figure 1 shows the logical symbol (and functional picture) of an "And-Or-Invert" gate that implements $F = (A(B + C))'$.

Estimate the activity factor, $\alpha_{F \rightarrow 1}$, for the output f , if $p(A = 1) = 1/2$, $p(B = 1) = 1/4$, and $p(C = 1) = 1/3$.

$$P(A \cdot (B+C)=1) = P(A=1) \cdot P(B+C=1)$$

$$= \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$$


$$\alpha_{F \rightarrow 1} = P(F=0) \cdot P(F=1)$$

$$= \frac{1}{4} \cdot \frac{3}{4}$$

$$= \frac{3}{16}$$

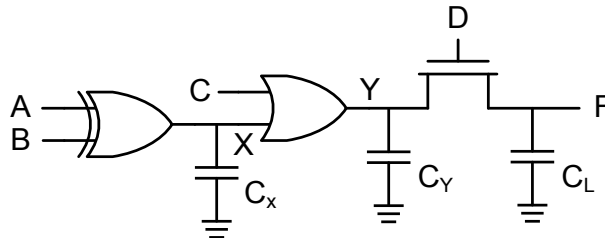Problem 2: Power and Energy

Consider the following circuit, with XOR, AND gates and one NMOS transistor.



$$P_{sw} = P_{sw,X} + P_{sw,Y} + P_{sw,F}$$

$$= 4.9 \cdot 10^{-7} + 2.3616 \cdot 10^{-7}$$

$$= 7.2616 \cdot 10^{-7} W$$

(a) What logic function is implemented by this circuit (inputs: A, B, C, and D)?

$$F = [(A \oplus B) + C] \cdot D$$

(b) Assume the probability of logic 1 for inputs: $p(A = 1) = 0.5$, $p(B = 1) = 0.5$, $p(C = 1) = 0.2$, $p(D = 1) = 0.3$, capacitance: $C_X = C_Y = 10$ fF, $C_L = 20$ fF, frequency $f = 100$ MHz, $V_{DD} = 1$ V, threshold voltage $V_{TN} = 0.2$ V, $V_{TP} = -0.3$ V. Calculate the average switching power P_{sw} of the circuit (logic gates and input D are powered from V_{DD}).

$$p(X=1) = P(A=1) \cdot P(B=0) + P(A=0) \cdot P(B=1) = \frac{1}{2} \cdot \frac{1}{2} + \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{2}$$

$$p(X=1) = \frac{1}{2}$$

$$\alpha_{X:0 \rightarrow 1} = \frac{1}{4}$$

$$\alpha_{X \rightarrow 1} = P(X=0) \cdot P(X=1) = \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$$

$$= P(X=0) \cdot (1 - P(X=0))$$

$$p(Y=1) = 0.6$$

$$\alpha_{Y:0 \rightarrow 1} = 0.24$$

$$P(Y=1) = P(X=1) \cdot P(C=0) + P(X=0) \cdot P(C=1) + P(X=1) \cdot P(C=1)$$

$$= \frac{1}{2} \cdot 0.8 + \frac{1}{2} \cdot 0.2 + \frac{1}{2} \cdot 0.2 = 0.6$$

$$\alpha_{Y \rightarrow 1} = P(Y=0) \cdot P(Y=1) = 0.4 \cdot 0.6$$

$$P_{sw,X} + P_{sw,Y} = 4.9 \cdot 10^{-7} W$$

$$P_{sw,X} + P_{sw,Y} = (\alpha_X \cdot C_X + \alpha_Y \cdot C_Y) \cdot V_{DD}^2 \cdot f$$

$$= \left(\frac{1}{4} \cdot 10 \cdot 10^{-15} + 0.24 \cdot 10 \cdot 10^{-15} \right) \cdot 1^2 \cdot 100 M = 4.9 \cdot 10^{-7} W$$

$$P(F=1) = 0.18$$

$$\alpha_{F:0 \rightarrow 1} = 0.1476$$

$$P(F=1) = P(Y=1) \cdot P(D=1) = 0.6 \cdot 0.3 = 0.18$$

$$P_{sw,F} = 2.3616 \cdot 10^{-7} W$$

$$\alpha \cdot C \cdot V_{DD} \cdot (V_{DD} - V_{TN}) \cdot f$$

$$\alpha_{F \rightarrow 1} = P(F=1) \cdot P(F=0) = 0.1476$$

$$P_{sw,F} = 0.1476 \cdot 20 f \cdot 1 \cdot (1 - 0.2) \cdot 100 M$$

XOR:

A	B	X
0	0	0
1	0	1
0	1	1
1	1	0

AND:

X	C	Y
0	0	0
1	0	1
0	1	1
1	1	1

charging

$$E_{\text{supply}} = C \cdot V_D = (V_0 - V_i)$$

$$E_{\text{cap}} = \frac{1}{2} C (V_0^2 - V_i^2)$$

$$E_{\text{heat}} = E_{\text{supply}} - E_{\text{cap}}$$

discharging

$$E_{\text{heat}} = E_{\text{cap}}$$

@ Node X

$$\text{charging } E_{\text{supply}} = 10 \text{ f} \cdot 1 \cdot (1-0) = 10 \text{ fJ}$$

$$E_{\text{cap}} = \frac{1}{2} \cdot 10 \text{ f} \cdot (1^2 - 0^2) = 5 \text{ fJ}$$

$$E_{\text{heat}} = 10 \text{ fJ} - 5 \text{ fJ} = 5 \text{ fJ}$$

$$\text{Discharging } E_{\text{heat}} = 5 \text{ fJ}$$

@ Node Y

$$\text{charging } E_{\text{supply}} = 10 \text{ f} \cdot 1 \cdot (1-0) = 10 \text{ fJ}$$

$$E_{\text{cap}} = \frac{1}{2} \cdot 10 \text{ f} \cdot (1^2 - 0^2) = 5 \text{ fJ}$$

$$E_{\text{heat}} = 10 \text{ fJ} - 5 \text{ fJ} = 5 \text{ fJ}$$

$$\text{Discharging } E_{\text{heat}} = 5 \text{ fJ}$$

@ Node L

$$\text{charging } E_{\text{supply}} = 20 \text{ f} \cdot 1 \cdot (1-0) = 16 \text{ fJ}$$

$$E_{\text{cap}} = \frac{1}{2} \cdot 20 \text{ f} \cdot (0.8^2 - 0^2) = 6.4 \text{ fJ}$$

$$E_{\text{heat}} = 16 \text{ fJ} - 6.4 \text{ fJ} = 9.6 \text{ fJ}$$

$$\text{Discharging } E_{\text{heat}} = 6.4 \text{ fJ}$$

(c) Calculate the heat energy dissipation for charging and discharging C_X , C_Y , and C_L .


Heat Energy	Charging	Discharging
Node X (C_X)	5 fJ	5 fJ
Node Y (C_Y)	5 fJ	5 fJ
Node F (C_L)	9.6 fJ	6.4 fJ
Total E_{heat}	19.6 fJ	16.4 fJ

Problem 3: CMOS Logic and Delay

(a) Implement the following function using static CMOS logic.

$$F = A(B + C)(D + E + F)$$

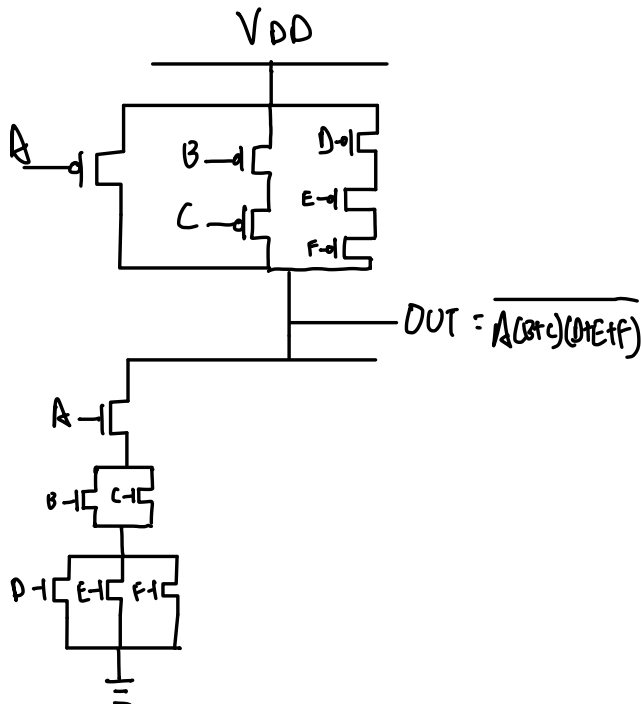(b) Assume output load capacitance $C_L = 50$ fF, and that transistors are sized such that the on-resistance of NMOS $R_N = 12$ k Ω , on-resistance of PMOS $R_P = 24$ k Ω . Calculate the **worst-case** low-to-high propagation delay t_{pLH} and the **best-case** high-to-low delay t_{pHL} . Assume ideal step-input switching.



$$\text{Worst } t_{pLH} = 8.28 \cdot 10^{-10} \text{ s}$$

$$\text{Best } t_{pHL} =$$

$$t_{pLH} = 0.69 \cdot 3R_P \cdot C_L = 0.69 \cdot 24 \text{ k} \cdot 50 \text{ fF} = 2.48 \cdot 10^{-9} \text{ s}$$

when there three PMOS $A = D, B \text{ or } C = 0$ and $D \text{ or } E \text{ or } F = 0$

$$t_{pHL} = 0.69 \cdot 3R_N \cdot C_L = 0.69 \cdot 12 \text{ k} \cdot 50 \text{ fF} = 1.242 \cdot 10^{-9} \text{ s}$$

we need $A = 1$
 $B \text{ or } C = 1$
 $D \text{ or } E \text{ or } F = 1$
to go low