

# $A[53.7] \text{ FO4}_{(1V)}, [183.02] E_{u(1V)}$ 4-bit Absolute Value Detector

G7 Team member: Chengming Li, Haowei Ge, Rui Yang and Zhuohao Chang

# Design Summary

- 1a) Circuit topology, 1b) Circuit Style
  - (2 to 1 Mux + Simplified Half Adder + 3bit MSB to LSB Comparator )
  - static CMOS, XOR, AND, and OR
  - Moderate Area, Regular and Intuitive design. Simplified Half Adder uses less logic gates than normal Half Adder
- 2) Sizing + Vdd optimization / Sizing impact
  - Delay increase: [50]% out of 50%
  - Energy reduction : [27.58]% out of 50%
- 3) Sizing + Vdd optimization /  $V_{DD}$  impact
  - Delay increase: [50]% out of 50%
  - Energy reduction : [40]% out of 50%
- 4) Sizing + Vdd optimization / combination impact
  - Delay increase: [50]% out of 50%
  - Energy reduction : [56.5]%

# Design Preview

- 1. **Decide the sign of given input** , i.e., compared input bit 3( $A_3$ ) with logic 0.

One input with  $A_3$  and another input connects to ground.


- 2. **Building a 3 bit 2's complement circuit**, decision done by the step 1.

Output 3-bit magnitude

- 3. Output from step 2 and **compared it with given threshold value(3-bit comparator)**.

# Design Topology & Reasoning

- Schematic

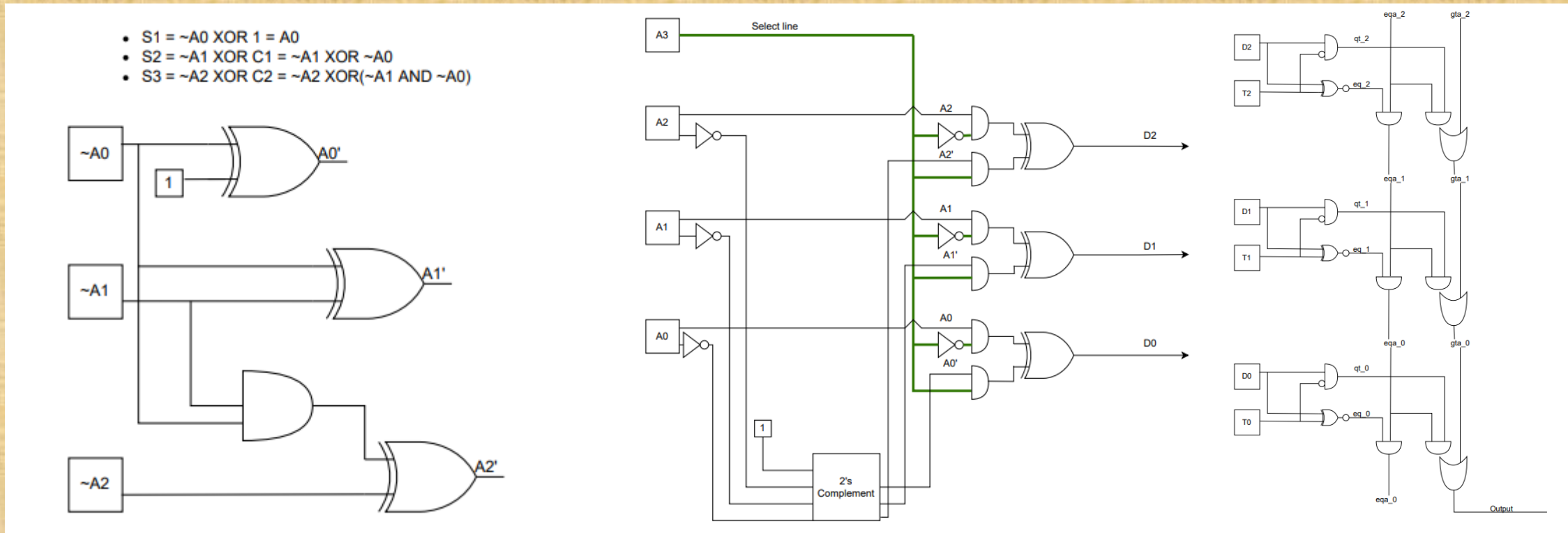


- Simplified Half Adder


2-1 Mux(2's Complement refers figure 1) 3-bit Comparator

# Design Topology (Continuing)


- AND gate can be implemented as below

 

- OR gate can be implemented as below

 

- XOR gate can be implemented as below

 



# Design Topology & Reasoning

- Reasoning


- This is an intuitive design, and we got ideas from combinational logic.
- Beyond that, we made a little improvement on the Half-Adder design, which uses less logic gates and so transistors. Thus, it saves energy from the design perspective.

- Other options

- We have considered the full adder, ripple adder, etc. But we thought it was not necessary to put a full adder into the design, since we were not designing an ALU to do a very complex calculation. And main goal of this design is saving energy and with less transistors


# Critical Path Analysis

- Highlight Critical Path

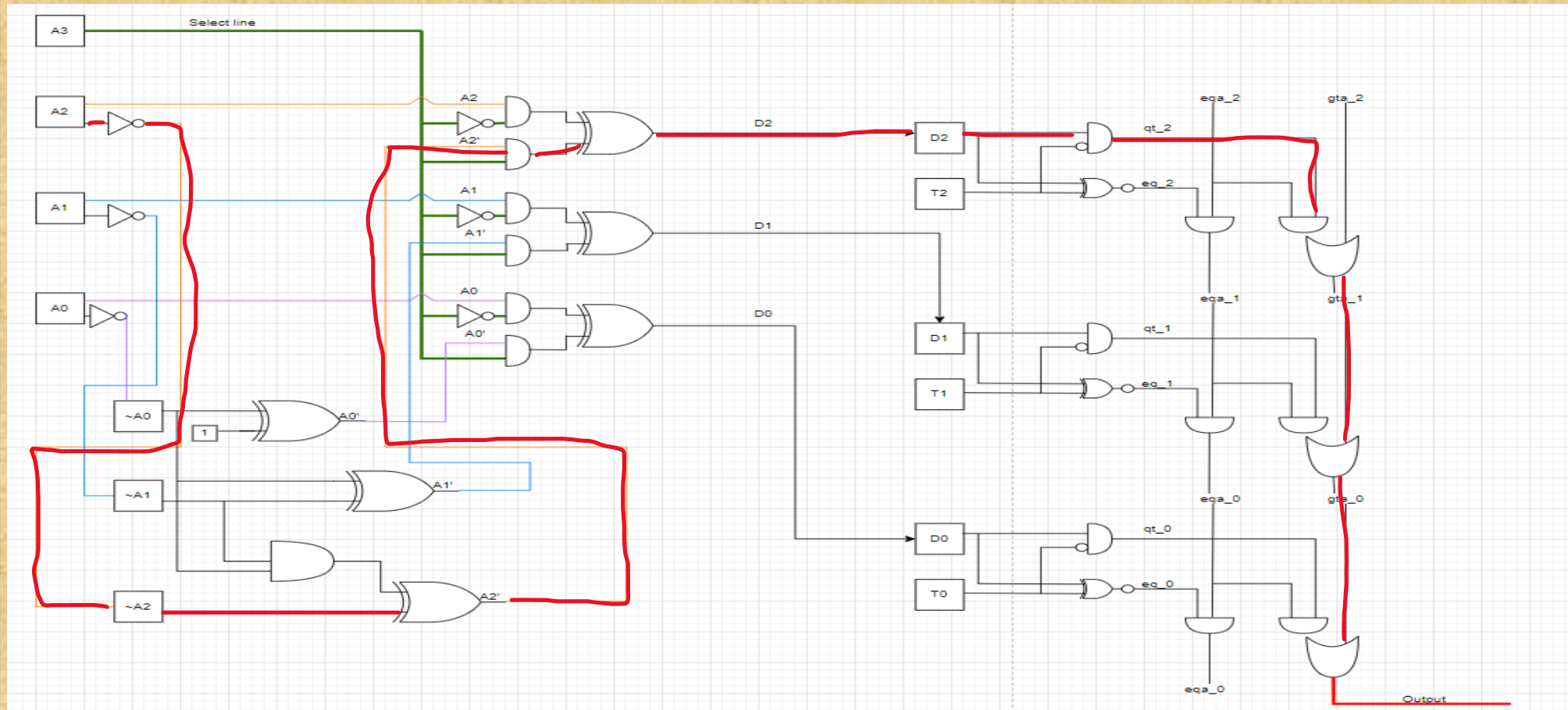
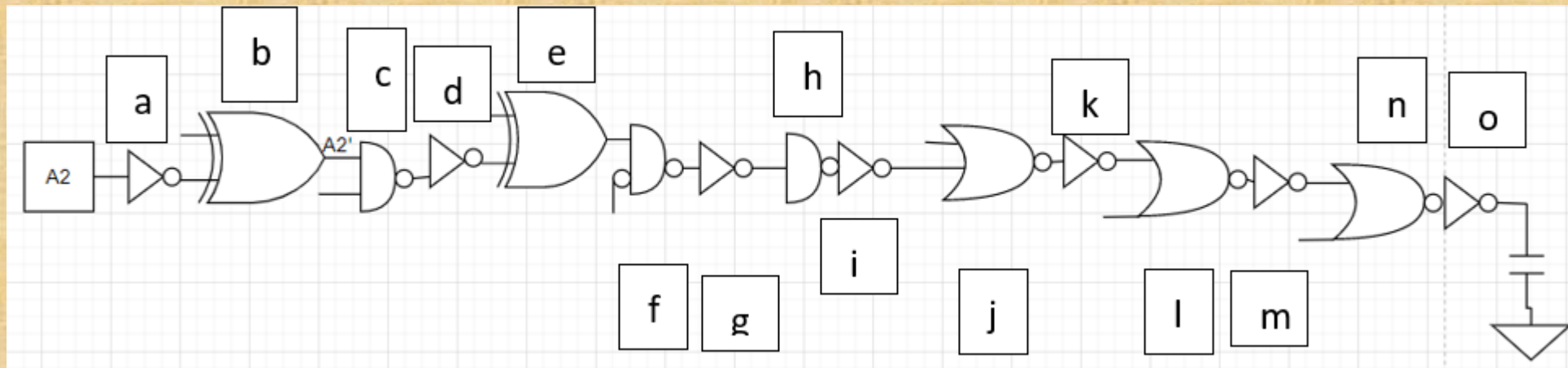
# Critical Path Gate Sizing Approach

- Show sizing optimization of the critical path



- Sizing of each stage :  $C_{in} = g \times C_{out}/f^*$

a = 1	b = 1.78	c = 0.79	d = 1.05	e = 1.88	f = 0.83	g = 1.11	h = 1.98
i = 2.64	j = 4.69	k = 5	l = 8.9	m = 9.49	n = 16.9	o = 18	



# Critical Path Gate Sizing Approach (Continuing)

- $C_{out} = 32 \quad C_{in} = 1$
- Parasitic delay:  $p_{XOR} = \frac{6.5 \times 4 + 4.3 \times 4}{6.5 + 4.3} = 4$ ;  $p_{NAND} = \frac{6.5 \times 2 + 4.3 \times 2}{6.5 + 4.3} = 2$ ;  $p_{NOR} = \frac{6.5 \times 2 + 4.3 \times 2}{6.5 + 4.3} = 2$
- Logic effort:  $g_{XOR} = \frac{6.5 \times 4 + 4.3 \times 4}{6.5 + 4.3} = 4$ ;  $g_{NAND} = \frac{6.5 + 4.3 \times 2}{6.5 + 4.3} = 1.4$ ;  $g_{NOR} = \frac{6.5 \times 2 + 4.3}{6.5 + 4.3} = 1.6$
- $G = 1 * 4 * 1.4 * 1 * 4 * 1.4 * 1 * 1.4 * 1 * 1.6 * 1 * 1.6 * 1 * 1.6 * 1 = 179.83$
- $B = 1$
- $H = 32 / 1 = 32$
- Path effort  $F = GHB = 179.83 * 32 * 1 = 5754.9$
- **Stage effort:  $f^* = \sqrt[15]{F} = 1.78$**
- Min delay  $= 15 \times f^* + (1 + 4 + 2 + 1 + 4 + 2 + 1 + 2 + 1 + 2 + 1 + 2 + 1 + 2 + 1) = \mathbf{53.7}$
- **$C_{tot} = 183.02$**
- **Energy  $= C_{tot} * V_{dd}^2 = 183.02 * 1^2$**

# Sizing & $V_{DD}$ Energy Minimization

- Sizing impact

- By using excel model provided in the lecture,  $E_{tot}$  drops down to **132.54**, as  $1.5 * \text{Delay}_{\min}$

stage	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	load		
size	1	1.20	1.49	1.84	2.27	2.78	3.37	4.04	4.77	5.48	6.08	6.36	5.93	4.16	0.00	32		
Energy	2.20	2.69	3.33	4.11	5.05	6.15	7.41	8.81	10.25	11.57	12.44	12.28	10.09	4.16	32.00		<b>Etot</b>	<b>132.54</b>

- Vdd impact

- $D_{\min} = \frac{K * V_{dd}}{(V_{dd} - 0.2)^2} = 53.64 = \frac{K * V_{dd}}{(V_{dd} - 0.2)^2}$
- $K = 34.33$
- $1.5 * D_{\min} = \frac{53.64 * V_{dd'}}{(V_{dd} - 0.2)^2}$
- $V_{dd'} = 0.775$
- $\text{Energy} = C_{tot} * V_{dd}^2 = 183.02 \times 0.775^2 = \mathbf{109.93}$

- Combination impact

- $\text{Energy} = C_{tot} * V_{dd}^2 = 132.54 \times 0.775^2 = \mathbf{79.61}$

# Sizing vs. $V_{DD}$ Optimization ?

- How did you decide about relative contribution of sizing and VDD in your overall delay increase?
  - Calculated energy consumption using either sizing optimization or Vdd optimization.
  - Estimated the energy reduction in these two methods.
  - Greater energy reduction is the better way to reduce energy in the design
- Vdd optimization is the better way for this design, since it reduces 40% energy when delay is 1.5 times minimum delay
- We end up **56.5%** energy reduction when both optimization are applied

# Discussion & Summary

- Three most important features of our design
  - 1. Simplified Half-Adder Circuit
  - 2. Intuitive Design
  - 3. 3bit Comparator, from MSB to LSB, using gt and eq signal.
- Given another chance, 3 things you would do different
  - 1. Trying using PTL
  - 2. Calculate other paths' delay
  - 3. We have little problem in our excel solver, as one of the stage effort is 0. But we can't figure out the cause of this problem. I think we could do it better if there is more time provided



Q&A